

FINAL EXAMINATION JANUARY 2016 SEMESTER

COURSE

ECB2173/EDB2013 - ELECTROMAGNETIC THEORY

DATE

: 29TH APRIL 2016 (FRIDAY)

TIME

: 9.00 AM – 12.00 NOON (3 hours)

INSTRUCTIONS TO CANDIDATES

- Answer ALL questions from the Question Booklet.
- 2. Begin **EACH** answer on a new page in the Answer Booklet.
- 3. Indicate clearly answers that are cancelled, if any.
- 4. Where applicable, show clearly steps taken in arriving at the solutions and indicate **ALL** assumption.
- 5. Do not open this Question Booklet until instructed.

Note:

- i. There are **FIVE (5)** pages in this Question Booklet including the cover page.
- ii. Smith chart will be provided.

Universiti Teknologi PETRONAS

1. a. An infinitely long line of charge with uniform charge density, ρ_l , is placed along the y-axis as shown in **FIGURE Q1**.

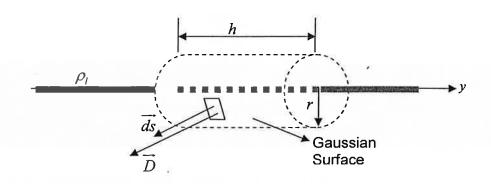


FIGURE Q1

i. Using the Gauss's law in differential form, derive its integral form.

[4 marks]

ii. Based on the integral form of Gauss's law, derive an expression for the electric field, \vec{E} , in free space due to the line charge given in **FIGURE Q1**.

[15 marks]

- b. Define the following:
 - i. Lorentz Force

[3 marks]

ii. Force on a Current-Carrying Conductor

[3 marks]

2. a. **FIGURE Q2** shows a plane wave propagation of **E**-field and **H**-field in both time and space. The direction of propagation is toward **+z**.

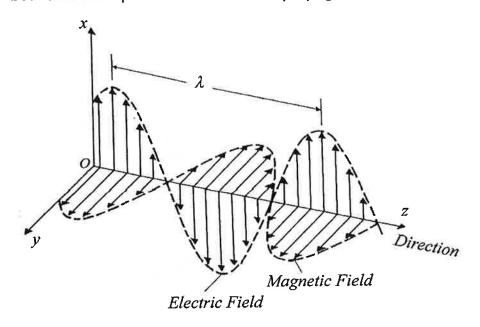


FIGURE Q2

i. State the FOUR (4) Maxwell equations.

[4 marks]

ii. Based on Maxwell equations and FIGURE Q2, derive the wave equations for both E and H-field and show that the vector fields are transverse.

[15 marks]

- b. A 10-MHz uniform plane wave is travelling in a nonmagnetic medium with $\mu=\mu_o$ and $\varepsilon_r=9$ where $\mu_0=4\pi\times 10^{-7}~H/m$, $\varepsilon_0=8.854\times 10^{-12}~F/m$.
 - i. Determine the phase velocity *v*.

[3 marks]

ii. Determine the wavenumber k.

[3 marks]

Two half-wave dipole antennas, each with impedance of $Z_L = 75~\Omega$, are connected in parallel through a pair of transmission lines, and the combination is connected to a feed transmission line, as shown in **FIGURE Q3**. All lines are lossless with characteristic impedance of $Z_0 = 50~\Omega$.

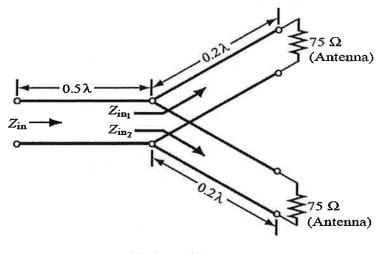


FIGURE Q3

Calculate Z_{in1} and Z_{in2} , the input impedance of the antenna-terminated line, at the parallel juncture as indicated in **FIGURE Q3**.

[3 marks]

b. Determine Z'_L , the effective load impedance of the feedline by combining Z_{in1} and Z_{in2} in parallel.

[3 marks]

c. Calculate input impedance Z_{in} , of the feedline.

[4 marks]

d. Assuming that all the transmission lines in **FIGURE Q3** have characteristic impedance of $Z_0 = 75\,\Omega$, determine the new value of input impedance $Z'_{\rm in}$ and construct a matching network to match to a $Z'_{\rm in}$ 50 Ω system.

[15 marks]

4. Consider the network shown in **FIGURE Q4**. All transmission lines in this network are lossless with $Z_0 = 50 \ \Omega$.

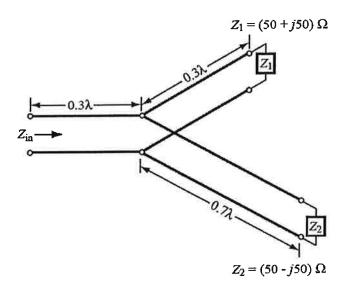


FIGURE Q4

a. Using the Smith Chart, determine the reflection coefficient at the load impedance, Z_1 .

[3 marks]

b. Using the Smith Chart, determine the reflection coefficient at the load impedance, \mathbb{Z}_2 .

[3 marks]

c. With the help of the Smith Chart, determine the input impedance Z_{in} , of the feed line.

[4 marks]

d. All the transmission lines shown in **FIGURE Q4** are replaced with half-wavelength transmission lines. Using the Smith Chart, determine the new input impedance $Z'_{\rm in}$.

[15 marks]

- END OF PAPER -

