

UNIVERSITI
TEKNOLOGI
PETRONAS

FINAL EXAMINATION JANUARY 2025 SEMESTER

COURSE : EFB1013 - CIRCUIT THEORY
DATE : 19 APRIL 2025 (SATURDAY)
TIME : 9.00 AM - 12.00 NOON (3 HOURS)

INSTRUCTIONS TO CANDIDATES

1. Answer **ALL** questions in the Answer Booklet.
2. Begin **EACH** answer on a new page in the Answer Booklet.
3. Indicate clearly answers that are cancelled, if any.
4. Where applicable, show clearly steps taken in arriving at the solutions and indicate **ALL** assumptions, if any.
5. **DO NOT** open this Question Booklet until instructed.

Note :

- i. There are **FIVE (5)** pages in this Question Booklet including the cover page .
- ii. **DOUBLE-SIDED** Question Booklet.

1. Kirchoff's laws and Thevenin/Norton theorems are techniques that can be used to analyze complex circuits.

a. A complex circuit is shown in **FIGURE Q1a**.

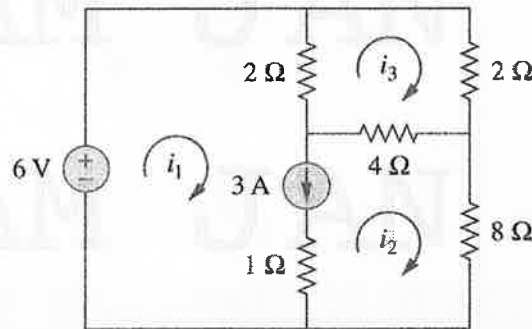


FIGURE Q1a

- i. State the condition for super-mesh and write down the mesh equations for the circuit using Kirchoff's voltage law.

[10 marks]

- ii. Determine all the mesh currents.

[8 marks]

- b. It is often desirable to ensure maximum power is transferred to the load (for example, a motor), as shown in **FIGURE Q1b**.

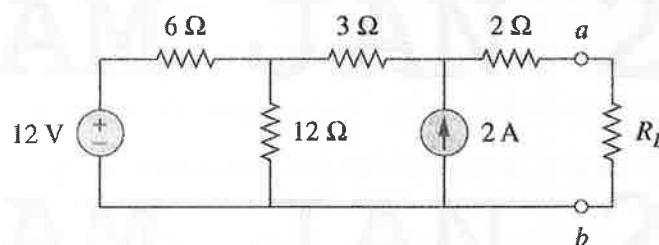


FIGURE Q1b

- i. Using Thevenin's theorem, find the equivalent circuit (R_{Th} and V_{Th}) to the left of the terminals a - b .

[8 marks]

- ii. Hence, state the value of R_L for maximum power transfer and determine the maximum power.

[4 marks]

2. Inductors are one of the important circuit elements that can store electrical energy in a magnetic field.

a. The current through a 0.1H inductor is $10te^{-5t}$ A. Find the voltage and the energy stored in it.

[7 marks]

b. The switch in the circuit shown in **FIGURE Q2** has been open for a long time. At $t = 0$, the switch is closed.

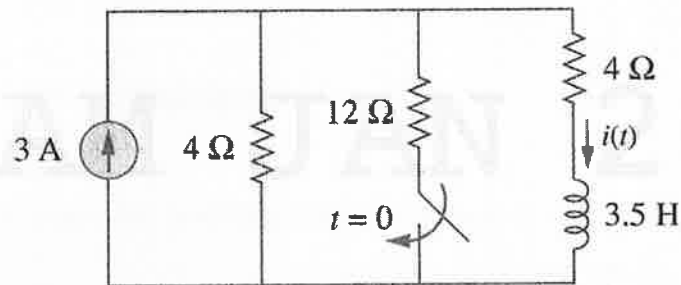


FIGURE Q2

i. With the switch opened, determine the inductor's initial current, $i(0)$.

[4 marks]

ii. With the switch closed, determine the inductor's final current, $i(\infty)$ and the time constant.

[8 marks]

iii. Evaluate whether the circuit is a source-free or step response circuit. Hence, determine the inductor's current, $i(t)$ for $t > 0$.

[6 marks]

iv. Discuss how the values of the current source and resistors in the circuit, affect the inductor's current, $i(t)$.

[5 marks]

3. The operational amplifier is an active circuit element that can be designed to perform mathematical operations. An op-amp circuit is shown in **FIGURE Q3**.

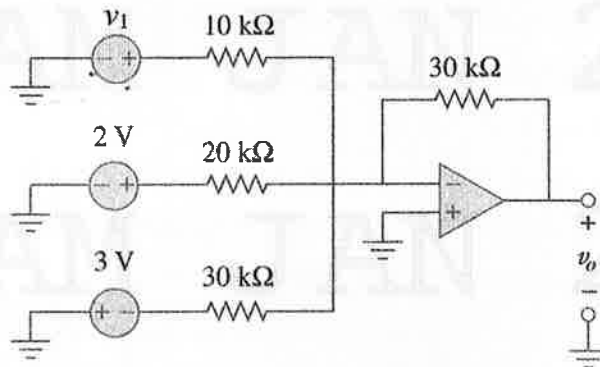


FIGURE Q3

- Identify the type of amplifier circuit and determine the output voltage, v_o , if $v_1 = 1\text{ V}$.
[10 marks]
- In order to obtain an output voltage, $v_o = 12\text{ V}$, what should be the new value of v_1 ?
[5 marks]
- If the resistance of the $30\text{-k}\Omega$ feedback resistor is doubled, discuss how this affects the output voltage, v_o .
[5 marks]

4. Phasors are an important tool for analyzing AC power circuits.

- a. Consider the circuit shown in **FIGURE Q4**.

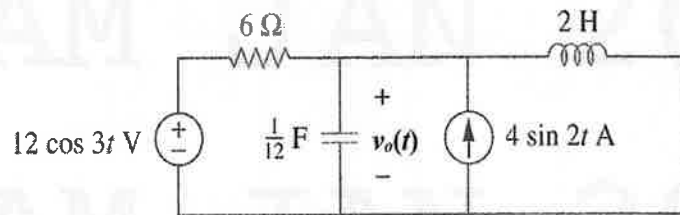


FIGURE Q4

- i. Construct the equivalent circuit for each frequency in phasor domain.

[4 marks]

- ii. Determine $v_o(t)$ using superposition theorem.

[8 marks]

- b. The voltage and current phasors, across a load is given as follows:-

$$\mathbf{V} = 110 \angle 85^\circ \text{ V rms}, \mathbf{I} = 0.4 \angle 15^\circ \text{ A rms}$$

Calculate the complex power, apparent power, real power, and reactive power.

[8 marks]

- END OF PAPER -

