



UNIVERSITI
TEKNOLOGI
PETRONAS

FINAL EXAMINATION MAY 2024 SEMESTER

COURSE : EEB2063/EFB2053 - MICROELECTRONIC CIRCUITS
DATE : 7 AUGUST 2024 (WEDNESDAY)
TIME : 9.00 AM - 12.00 NOON (3 HOURS)

INSTRUCTIONS TO CANDIDATES

1. Answer **ALL** questions in the Answer Booklet.
2. Begin **EACH** answer on a new page in the Answer Booklet.
3. Indicate clearly answers that are cancelled, if any.
4. Where applicable, show clearly steps taken in arriving at the solutions and indicate **ALL** assumptions, if any.
5. **DO NOT** open this Question Booklet until instructed.

Note :

- i. There are **SIX (6)** pages in this Question Booklet including the cover page and appendix.
- ii. **DOUBLE-SIDED** Question Booklet.

1. Consider a typical BJT amplifier connected to an active load as shown in **FIGURE Q1**. Assume that the circuit has a supply of $V^+ = 5\text{ V}$ and has the following transistor parameters: $I_{S0} = I_{S1} = I_{S2} = 1.5 \times 10^{-12}\text{ A}$ and $V_{AN} = V_{AP} = 120\text{ V}$.

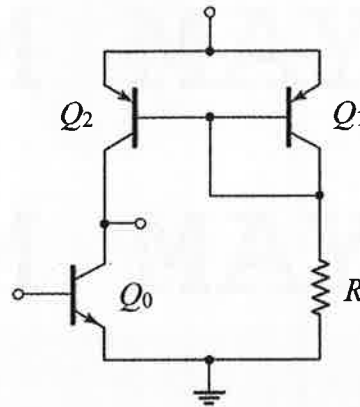


FIGURE Q1

- Redraw the circuit in **FIGURE Q1** and label all components, input v_1 , output v_O , current I_{REF} , and all other voltages and currents. Show clearly the current directions and terminal polarities. [6 marks]
- Referring to the sketch in **part (a)**, identify the elements that form the active load circuit, the transistor which is the active load driver and the transistor which functions as amplifier. [5 marks]
- Let $I_{REF} = I_S \exp\left(\frac{V_{EB2}}{V_T}\right)$. Determine the value of v_{EB2} and R such that $I_{REF} = 0.6\text{ mA}$. [6 marks]
- Assuming the following equation for the BJT amplifier with active load, evaluate the value of the input voltage, v_1 , to produce $v_{CE0} = v_{EC2}$.

$$I_{S0} \left[\exp\left(\frac{v_1}{V_T}\right) \right] \left(1 + \frac{v_{CE0}}{V_{AN}} \right) = I_{REF} \times \frac{\left(1 + \frac{v_{EC2}}{V_{AP}} \right)}{\left(1 + \frac{v_{EB2}}{V_{AP}} \right)}$$

[7 marks]

2. A differential amplifier is a fundamental building block of analog circuits commonly used as the input stage of an op-amp. **FIGURE Q2** shows a differential amplifier with the following transistor parameters: $\beta = 90$, $V_{BE(on)} = 0.75\text{ V}$, and $V_A = \infty$.

- a. For $v_1 = v_2 = 0$, find I_{C1} , I_{C2} , I_E , V_{CE1} and V_{CE2} .

[10 marks]

- b. Determine the maximum and minimum values of the common-mode input voltage, v_{cm} .

[6 marks]

- c. Calculate the differential-mode gain, A_d , for a one-sided output at the collector of Q_2 .

[8 marks]

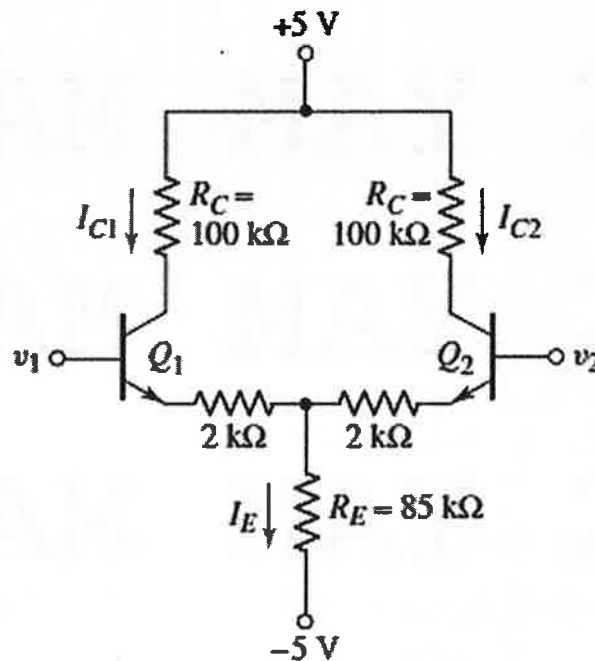


FIGURE Q2

3. **FIGURE Q3** shows an example of a shunt-series feedback circuit. A signal proportional to the output current is fed back to the shunt connection at the base of Q_1 . However, the circuit may be used as a voltage amplifier. Assume transistor parameters of $h_{FE} = 110$, $V_{BE(on)} = 0.65$ V, and $V_A = \infty$.

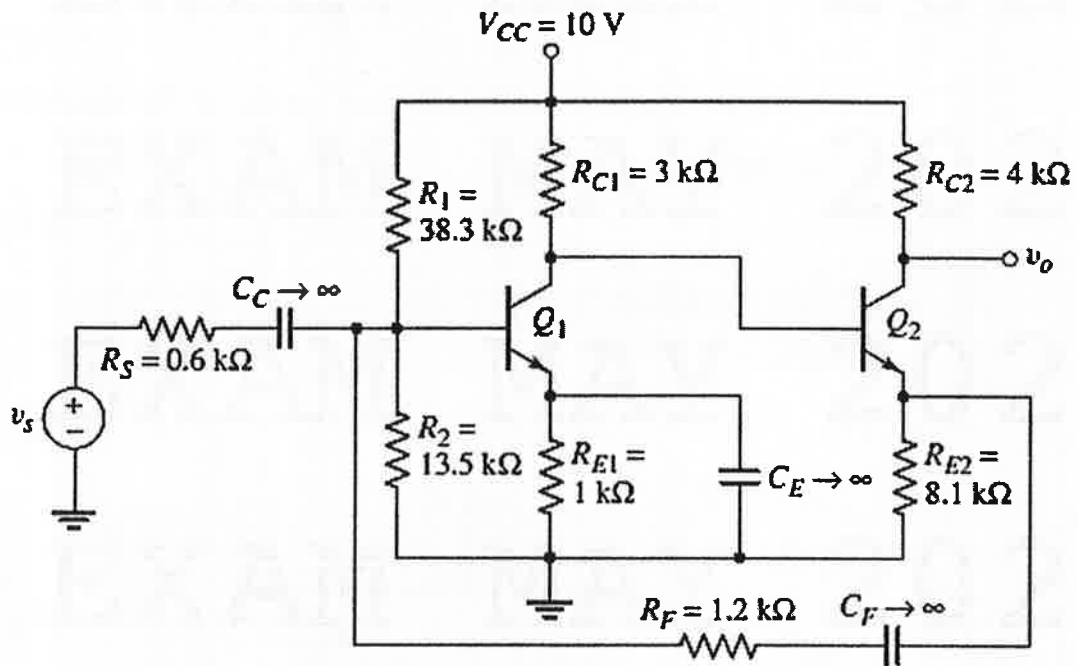


FIGURE Q3

- a. Construct a small-signal equivalent circuit of the shunt-series feedback circuit. [10 marks]

- b. For the input of transistor Q_1 , analyze the Thevenin equivalent resistance, R_{TH} , and Thevenin equivalent voltage, V_{TH} . [6 marks]

- c. If $R_{TH} = 9.98$ kΩ and $V_{TH} = 2.606$ V, determine the parameters I_{C1} , V_{C1} , $r_{\pi 1}$ and g_{m1} for transistor Q_1 . [10 marks]

4. a. Construct a Wien-bridge oscillator circuit and label completely the components. Identify in the sketch, the components for parallel and series impedances, Z_p and Z_s . Explain the functions of the different sub-systems in the Wien-bridge circuit.

[10 marks]

- b. State the equation for the loop gain $T(s)$ and define the amplifier gain A and feedback transfer function $\beta(s)$. Derive the equations for the impedances Z_p and Z_s .

[8 marks]

- c. The loop gain is given by:

$$T(j\omega_o) = \left(1 + \frac{R_2}{R_1}\right) \left[\frac{1}{3 + j\omega_o RC + (1/j\omega_o RC)} \right]$$

Show how the oscillation frequency ω_o is derived from the above equation and the condition for sustained oscillations. Derive the frequency ω_o .

[4 marks]

- d. Show how the relationship between resistors R_1 and R_2 is derived from the equation in **part (c)** for loop gain and the Barkhausen condition and state the relationship.

[4 marks]

- END OF PAPER -

APPENDIX I
KEY FORMULAE

Bipolar Junction Transistor (BJT)

DC current gain	$I_C = \beta I_B$
Transistor currents	$I_E = I_B + I_C$
Transistor emitter current	$I_E = (\beta + 1) I_B$
Internal emitter resistance	$r_e = \frac{26\text{mV}}{I_E}$
DC Current Ratio	$\alpha = \frac{I_C}{I_E}$
	$\beta = \frac{I_C}{I_B}$
	$\beta = \frac{\alpha}{1-\alpha} ; \alpha = \frac{\beta}{\beta+1}$
Transconductance	$g_m = \frac{I_C}{V_T} ; V_T = 26 \text{ mV}$
Small-signal Input Resistance between Base and Emitter	$r_\pi = \frac{\beta}{g_m}$
Early-Effect Resistance	$r_o = \frac{V_A}{I_C}$
Small-Signal Voltage Gain	$A_v = \frac{v_o}{v_i} ; G_v = \frac{v_o}{v_{sig}}$
Small-Signal Current Gain	$A_i = \frac{i_o}{i_i}$
Small-Signal Input and Output Impedances	$Z_i = \frac{V_i}{I_i} ; Z_o = \frac{V_o}{I_o}$
BJT Capacitances	$C_\mu = \frac{C_{\mu 0}}{\left(1 + \frac{V_{CB}}{V_{0c}}\right)^{m_{CKJ}}} ; C_{je} = 2C_{je0} ;$ $C_{de} = \tau_F g_m$ $C_\pi = C_{je} + C_{de}$